Wencong Huang (Team Member A)

Jared Orange (Team Member B),

Marcos Buznego (Team Member C),

CS 2200: Theory of Computer Science

HW 2

September 20th 2018

Problem 1

```
load And.hdl,
output-file And.out,
compare-to And.cmp,
output-list a%B3.1.3 b%B3.1.3 out%B3.1.3;
set a 0,
set b 0,
eval,
output;
set a 0,
set b 1,
eval,
output;
set a 1,
set b 0,
eval,
output;
set a 1,
set b 1,
eval,
output;
```

			N	ot.cmp	
1		in	-1	out	Дel
2	1	0		1	¤€
3	\perp	1		0	¤€
4					

```
6 /**μθ
7 ** Not gate:μθ
8 ** out = not inμθ
9 **/μθ
10 μθ
11 CHIP Not {μθ
12 ····IN in;μθ
13 ····OUT out;μθ
14 μθ
15 ····PARTS:μθ
16 ····// Put your code here:μθ
17 ····Nand(a=in, b=in, out=out);μθ
18 }μθ
```

```
10 load Not.hdl, ##
10 output-file Not.out, ##
11 output-list in%B3.1.3 out%B3.1.3; ##
12 eval, ##
13 output; ##
14 ##
15 set in 1, ##
16 eval, ##
17 output; ##
```

```
    Or.cmp

    1
    a
    b
    out
    4

    2
    0
    0
    0
    4

    3
    0
    1
    1
    1
    4

    4
    1
    0
    1
    1
    4

    5
    1
    1
    1
    1
    1
    4
```

```
load Or.hdl,
output-file Or.out,
compare-to Or.cmp,
output-list a%B3.1.3 b%B3.1.3 out%B3.1.3;
set a 0,
set b 0,
eval,
output;
set a 0,
set b 1,
eval,
output;
set a 1,
set b 0,
eval,
output;
set a 1,
set b 1,
eval,
output;
```

			Χα	or.cmp			
1	П	a	1	b	-1	out	Щel
2	\perp	0	\perp	0	\perp	0	¤€
3	\perp	0	\perp	1	\perp	1	¤€
4	\perp	1	\perp	0	-1	1	¤€
5	Т	1	Т	1	-1	0	¤€
6							

```
* Exclusive-or gate: # ፡

* * out = not (a == b) # ፡

* * out = not (a == b) # ፡

* */# ፡

** CHIP Xor {# ፡

** OUT out; # ፡

** PARTS: # ፡

** Not(in=a, out=aNot); # ፡

** Not(in=b, out=bNot); # ፡

** And(a=aNot, b=b, out=out1); # ፡

** Or(a=out1, b=out2, out=out); # if in the cout2, out=out1); # if in the cout2, out=out2); # if in the cout2, * in the cout2,
```

```
load Xor.hdl,
output-file Xor.out,
compare-to Xor.cmp,
output-list a%B3.1.3 b%B3.1.3 out%B3.1.3;
set a 0,™
set b 0,¤
eval,
output;
set a 0,¤⊲
set b 1,¤
eval,
output; #
set a 1,™
set b 0, 🗵
eval,
output;
set a 1,
set b 1,™
eval,
output;
```

```
Мих.стр
a
         b
                 sel
                          out
                 0
0
         0
                           0
0
         0
                  1
                           0
0
         1
                  0
                           0
0
         1
                 1
                           1
1
         0
                  0
                           1
1
         0
                  1
                           0
1
         1
                  0
                           1
1
         1
                  1
                           1
```

```
load Mux.hdl,
output-file Mux.out,
compare-to Mux.cmp,
output-list a%B3.1.3 b%B3.1.3 sel%B3.1.3 out%B3.1.3;
set a 0,
set b 0,
set sel 0,
eval,
output;
set sel 1,
eval,
output;
set a 0,
set b 1,
set sel 0,
eval,
output;
set sel 1,
eval,
output;
set a 1,
set b 0,
set sel 0,
eval,
output;
set sel 1,
eval,
```

```
39 output; 4
40 4
41 set a 1, 4
42 set b 1, 4
43 set sel 0, 4
44 eval, 4
45 output; 4
46 4
47 set sel 1, 4
48 eval, 4
49 output; 4
```

	And16.cmp		
1	a	b	out ∉
2	0000000000000000	0 00000000000000000	0000000000000000
3	0000000000000000	0 1111111111111111	. 0000000000000000
4	1111111111111111	1 11111111111111111	111111111111111
5	101010101010101	0 0101010101010101	. 0000000000000000
6	001111001100001	1 0000111111110000	0000110011000000
7	000100100011010	0 1001100001110110	0001000000110100

```
* 16-bit bitwise And:
 * for i = 0..15: out[i] = (a[i] and b[i])
 */
CHIP And16 {
    IN a[16], b[16];
    OUT out[16];
   PARTS:
 // Put your code here:
 And(a=a[0], b=b[0], out=out[0]);
 And(a=a[1], b=b[1], out=out[1]);
 And(a=a[2], b=b[2], out=out[2]);
 And(a=a[3], b=b[3], out=out[3]);
 And(a=a[4], b=b[4], out=out[4]);
 And(a=a[5], b=b[5], out=out[5]);
 And(a=a[6], b=b[6], out=out[6]);
 And(a=a[7], b=b[7], out=out[7]);
 And(a=a[8], b=b[8], out=out[8]);
  And(a=a[9], b=b[9], out=out[9]);
  And(a=a[10], b=b[10], out=out[10]);
 And(a=a[11], b=b[11], out=out[11]);
 And(a=a[12], b=b[12], out=out[12]);
 And(a=a[13], b=b[13], out=out[13]);
 And(a=a[14], b=b[14], out=out[14]);
 And(a=a[15], b=b[15], out=out[15]);
```

```
load And16.hdl,
output-file And16.out,
compare-to And16.cmp,
output-list a%B1.16.1 b%B1.16.1 out%B1.16.1;
eval.
output;
set b %B11111111111111111,
eval,
output;
set a %B11111111111111111,
eval,
output;
set a %B1010101010101010,
set b %B0101010101010101,
eval,
output;
set a %B0011110011000011,
set b %B0000111111110000,
eval,
output;
set a %B0001001000110100,
set b %B1001100001110110,
eval,
output;
```

```
DMux.cmp
in
        sel
                  a
0
                           0
                  0
0
         1
                  0
                           0
1
1
         1
                  0
                            1
```

```
7 * Demultiplexor:μθ
8 * {a, b} = {in, 0} if sel == 0μθ
9 * {0, in} if sel == 1μθ
10 */μθ
11 μθ
12 CHIP DMux {μθ
13 ···IN in, sel;μθ
14 ···OUT a, b;μθ
15 μθ
16 ···PARTS:μθ
17 ···// Put your code here:μθ
18 ···Not(in=sel, out=notsel);μθ
19 ···And(a=in, b=sel, out=b);μθ
20 ···And(a=in, b=notsel, out=a);μθ
21 }μθ
```

```
load DMux.hdl,
    output-file DMux.out,
8 compare-to DMux.cmp,
    output-list in%B3.1.3 sel%B3.1.3 a%B3.1.3 b%B3.1.3;
   set in 0,™
12 set sel 0, X
13 eval,
14 output;
16 set sel 1, #
17 eval,¤
18 output;¤↵
20 set in 1, 14
21 set sel 0, X
22 eval,¤
   output;
25 set sel 1,¤
26 eval,
27 output;
```

	Not16.cmp			
1	in	Ī	out	=
2	00000000000000000	1	11111111111111111	$\left \in \right $
3	11111111111111111	1	0000000000000000	$\left \in\right $
4	1010101010101010	1	0101010101010101	$\left \in \right $
5	0011110011000011	1	1100001100111100	$\left \in \right $
6	0001001000110100	Ī	1110110111001011	$\overline{ }$

```
* 16-bit Not:
* for i=0..15: out[i] = not in[i]
CHIP Not16 {
    IN in[16];
   OUT out[16];
    PARTS:
   Nand(a=in[0], b=in[0], out=out[0]);
    Nand(a=in[1], b=in[1], out=out[1]);
   Nand(a=in[2], b=in[2], out=out[2]);
   Nand(a=in[3], b=in[3], out=out[3]);
    Nand(a=in[4], b=in[4], out=out[4]);
    Nand(a=in[5], b=in[5], out=out[5]);
    Nand(a=in[6], b=in[6], out=out[6]);
    Nand(a=in[7], b=in[7], out=out[7]);
    Nand(a=in[8], b=in[8], out=out[8]);
   Nand(a=in[9], b=in[9], out=out[9]);
    Nand(a=in[10], b=in[10], out=out[10]);
    Nand(a=in[11], b=in[11], out=out[11]);
    Nand(a=in[12], b=in[12], out=out[12]);
    Nand(a=in[13], b=in[13], out=out[13]);
    Nand(a=in[14], b=in[14], out=out[14]);
   Nand(a=in[15], b=in[15], out=out[15]);
```

```
load Not16.hdl,
output-file Not16.out,
compare-to Not16.cmp,
output-list in%B1.16.1 out%B1.16.1;
eval,
output;
set in %B1111111111111111,
eval,
output;
set in %B1010101010101010,
eval,
output;
set in %B0011110011000011,
eval,
output;
set in %B0001001000110100,
eval,
output;
```

	Or16.cmp		×			
1	a	Ī	b	Ī	out	₹
2	00000000000000000	Τ	00000000000000000	1	00000000000000000	₽
3	00000000000000000	1	11111111111111111	1	11111111111111111	€I
4	1111111111111111	1	11111111111111111	1	11111111111111111	ĕ
5	1010101010101010	1	0101010101010101	1	11111111111111111	€I
6	0011110011000011	Ī	0000111111110000	٦	0011111111110011	€I
7	0001001000110100	Ī	1001100001110110	٦	1001101001110110	↵

```
* 16-bit bitwise Or:
* for i = 0..15 out[i] = (a[i] \text{ or } b[i])
CHIP Or16 {
   IN a[16], b[16];
   OUT out[16];
   PARTS:
Put your code here:
 Or(a=a[0], b=b[0], out=out[0]);
 Or(a=a[1], b=b[1], out=out[1]);
 Or(a=a[2], b=b[2], out=out[2]);
 Or(a=a[3], b=b[3], out=out[3]);
 Or(a=a[4], b=b[4], out=out[4]);
 Or(a=a[5], b=b[5], out=out[5]);
 Or(a=a[6], b=b[6], out=out[6]);
 Or(a=a[7], b=b[7], out=out[7]);
 Or(a=a[8], b=b[8], out=out[8]);
 Or(a=a[9], b=b[9], out=out[9]);
 Or(a=a[10], b=b[10], out=out[10]);
 Or(a=a[11], b=b[11], out=out[11]);
 Or(a=a[12], b=b[12], out=out[12]);
 Or(a=a[13], b=b[13], out=out[13]);
 Or(a=a[14], b=b[14], out=out[14]);
 Or(a=a[15], b=b[15], out=out[15]);
```

```
load Or16.hdl,
output-file Or16.out,
compare-to Or16.cmp,
output-list a%B1.16.1 b%B1.16.1 out%B1.16.1;
eval,
output;
set b %B1111111111111111,
eval,
output;
set a %B11111111111111111,
eval,
output;
set a %B1010101010101010,
set b %B0101010101010101,
eval,
output;
set a %B0011110011000011,
set b %B0000111111110000,
eval,
output;
set a %B0001001000110100,
set b %B1001100001110110,
eval,
output;
```

```
/**
* 8-way Or:
* out = (in[0] or in[1] or ... or in[7])
*/¤
CHIP Or8Way {#4
•••• IN in[8];
OUT out;
   PARTS: ¤
Put your code here:
Or(a=in[0], b=in[1], out=c1);
Or(a=in[2], b=in[3], out=c2);
••••Or(a=in[4], b=in[5], out=c3);
••••Or(a=in[6], b=in[7], out=c4);
Or(a=c1, b=c2, out=c5);
or(a=c3, b=c4, out=c6);
Or(a=c5, b=c6, out=out);
```

```
load Or8Way.hdl,
output-file Or8Way.out,
compare-to Or8Way.cmp,
output-list in%B2.8.2 out%B2.1.2;
set in %B00000000,
eval,¤
output; #4
set in %B111111111,¤≪
eval,¤
output; #4
set in %B00010000,¤⊲
eval,¤
output;¤↵
set in %B00000001,¤≪
eval,¤
output; #4
set in %B00100110,
eval,
output;
```

```
DMux4Way.cmp
| in
         sel
                          b
                                        d
                  a
          00
                  0
                                 0
                                        0
   0
                          0
   0
          01
                  0
                          0
                                 0
                                        0
  0
          10
                  0
                          0
                                 0
                                        0
  0
          11
                  0
                          0
                                 0
                                        0
  1
          00
                          0
                  1
                                 0
                                        0
                          1
   1
          01
                  0
                                        0
                                 0
   1
          10
                  0
                          0
                                 1
                                        0
          11
                  0
                          0
                                 0
                                        1
```

```
load DMux4Way.hdl,
output-file DMux4Way.out,
compare-to DMux4Way.cmp,
output-list in%B2.1.2 sel%B2.2.2 a%B2.1.2 b%B2.1.2 c%B2.1.2 d%B2.1.2;
set in 0,
set sel %B00,
eval,
output;
set sel %B01,
eval,
output;
set sel %B10,
eval,
output;
set sel %B11,
eval,
output;
set in 1,
set sel %B00,
eval,
output;
set sel %B01,
eval,
output;
set sel %B10,
eval,
```

```
39 output; 4
40 4
41 set sel %B11, 4
42 eval, 4
43 output; 4
```

		ı	DM	lux8Wa	y.cm	ıр															
1	i	in	ı	sel	Т	a	Т	b	Т	С	Τ	d	Τ	e	Τ	f	Τ	g	Τ	h	Į d
2	-1	0	Π	000	Т	0	Т	0	Т	0	Т	0	Т	0	Т	0	Τ	0	Т	0	₽
3	-1	0	ı	001	1	0	Т	0	Т	0	Т	0	Т	0	Т	0	Τ	0	Т	0	₽
4	-1	0	ı	010	1	0	1	0	Т	0	Τ	0	Τ	0	Т	0	Τ	0	1	0	$ \in$
5	-1	0	ı	011	1	0	Т	0	Т	0	Τ	0	1	0	1	0	\mathbf{I}	0	1	0	$ \in$
6	-1	0	l	100	1	0	Т	0	Т	0	\perp	0	1	0	1	0	\perp	0	1	0	$ \in$
7	-1	0	l	101	1	0	Т	0	Т	0	Т	0	1	0	1	0	1	0	Т	0	I∉I
8	-1	0	l	110	1	0	Т	0	Т	0	Τ	0	1	0	1	0	Τ	0	Т	0	$ \in$
9	-1	0	l	111	1	0	Т	0	Т	0	\perp	0	1	0	1	0	\perp	0	1	0	$ \in$
10	-1	1	l	000	1	1	Т	0	Т	0	Τ	0	1	0	Т	0	Τ	0	Т	0	I∉I
11	-1	1		001	1	0	Т	1	Т	0	Т	0	1	0	Т	0	\perp	0	Т	0	Į.
12	-1	1	l	010	1	0	Т	0	Т	1	Т	0	1	0	Т	0	1	0	Т	0	I ∉I
13	-1	1	l	011	1	0	Т	0	Т	0	Τ	1	1	0	Т	0	Τ	0	Т	0	I∉I
14	-1	1	l	100	1	0	Т	0	Т	0	Τ	0	1	1	1	0	Τ	0	1	0	$ \in$
15	-	1	I	101	1	0	1	0	1	0	1	0	1	0	1	1	1	0	1	0	₽
16		1	I	110	1	0	1	0	1	0		0	-	0	Τ	0	T	1	Τ	0	₽
17	T	1	Ī	111	Τ	0	Τ	0	Τ	0	Ι	0	Τ	0	Τ	0	Τ	0	Τ	1	₽

```
set sel %B111,
   eval,
    output;
44 set in 1,
45 set sel %B000,
46 eval,
    output;
   set sel %B001,
   eval,
    output;
   set sel %B010,
∠4 eval,
    output;
57 set sel %B011,
58 eval,
    output;
   set sel %B100,
   eval,
    output;
    set sel %B101,
   eval,
    output;
   set sel %B110,
    eval,
```

```
71 output; 4
72 4
73 set sel %B111, 4
74 eval, 4
75 output; 4
76
```

	Мих16.стр						
1	l a	1	b	ī	sel	out	Į jie
2	000000000000000000	000000	0000000000	ï	0	00000000000000000	μĸ
3	00000000000000000	000000	0000000000	Ī	1	00000000000000000	Д÷
4	00000000000000000	000100	1000110100	Τ	0	00000000000000000	Щ÷
5	00000000000000000	000100	1000110100	Т	1	0001001000110100	Ц÷
6	1001100001110110	000000	0000000000	Τ	0	1001100001110110	Д÷
7	1001100001110110	000000	0000000000	Т	1	00000000000000000	Ц÷
8	1010101010101010	010101	0101010101	Ī	0	1010101010101010	Д÷
9	1010101010101010	010101	0101010101	T	1	0101010101010101	Д÷

```
* 16-bit multiplexor:
 * for i = 0..15 out[i] = a[i] if sel == 0
                          b[i] if sel == 1
 */¤<
CHIP Mux16 {
    IN a[16], b[16], sel;
   OUT out[16];
   PARTS: IK
   // Put your code here:
   Mux(a=a[0], b=b[0], sel=sel, out=out[0]);
   Mux(a=a[1], b=b[1], sel=sel, out=out[1]);
   Mux(a=a[2], b=b[2], sel=sel, out=out[2]);
   Mux(a=a[3], b=b[3], sel=sel, out=out[3]);
   Mux(a=a[4], b=b[4], sel=sel, out=out[4]);
   Mux(a=a[5], b=b[5], sel=sel, out=out[5]);
   Mux(a=a[6], b=b[6], sel=sel, out=out[6]);
   Mux(a=a[7], b=b[7], sel=sel, out=out[7]);
   Mux(a=a[8], b=b[8], sel=sel, out=out[8]);
   Mux(a=a[9], b=b[9], sel=sel, out=out[9]);
   Mux(a=a[10], b=b[10], sel=sel, out=out[10]);
   Mux(a=a[11], b=b[11], sel=sel, out=out[11]);
   Mux(a=a[12], b=b[12], sel=sel, out=out[12]);
   Mux(a=a[13], b=b[13], sel=sel, out=out[13]);
   Mux(a=a[14], b=b[14], sel=sel, out=out[14]);
   Mux(a=a[15], b=b[15], sel=sel, out=out[15]);
```

```
load Mux16.hdl,
   output-file Mux16.out,
8 compare-to Mux16.cmp,
   output-list a%B1.16.1 b%B1.16.1 sel%D2.1.2 out%B1.16.1;
   set a 0,™
12 set b 0, ⊯
13 set sel 0,
14 eval,
   output;
17 set sel 1,¤√
18 eval,
   output;
22 set b %B0001001000110100,
23 set sel 0,
24 eval,
25 output; #
   set sel 1,
28 eval,
   output;
   set a %B1001100001110110, 🖂
33 set sel 0,1
34 eval,
   output;
```

```
37 set sel 1, ##

38 eval, ##

39 output; ##

40 ##

41 set a %B1010101010101010, ##

42 set b %B0101010101010101, ##

43 set sel 0, ##

44 eval, ##

45 output; ##

46 ##

47 set sel 1, ##

48 eval, ##

49 output;
```

Mux4Way16.cmp					
a	l b			sel	out
00000000000000000	00000000000000000	00000000000000000	00000000000000000	00	000000000000000000
00000000000000000	00000000000000000	00000000000000000	00000000000000000	01	000000000000000000
00000000000000000	00000000000000000	00000000000000000	00000000000000000	10	000000000000000000
00000000000000000	00000000000000000	00000000000000000	00000000000000000	11	000000000000000000
0001001000110100	1001100001110110	1010101010101010	0101010101010101	00	0001001000110100
0001001000110100	1001100001110110	1010101010101010	0101010101010101	01	1001100001110110
0001001000110100	1001100001110110	1010101010101010	0101010101010101	10	1010101010101010
0001001000110100	1001100001110110	1010101010101010	0101010101010101	11	0101010101010101

```
load Mux4Way16.hdl,
   output-file Mux4Way16.out,
   compare-to Mux4Way16.cmp,
   output-list a%B1.16.1 b%B1.16.1 c%B1.16.1 d%B1.16.1 sel%B2.2.2 out%B1.16.1;
   set a 0,
   set b 0,
   set d 0,
   eval,
   output;
   eval,
   output;
   output;
   eval,
   output;
   set a %B0001001000110100,
   set b %B1001100001110110,
   set c %B1010101010101010,
34 set d %B010101010101010101,
```

```
35 set sel 0,4
36 eval,4
37 output;4
38 4
39 set sel 1,4
40 eval,4
41 output;4
42 4
43 set sel 2,4
44 eval,4
45 output;4
46 4
47 set sel 3,4
48 eval,4
49 output;4
50
```

	Mux8Way16.cmp							
1	a			l d	e			
2	00000000000000000	0000000000000000	00000000000000000	00000000000000000	00000000000000000	00000000000000000	00000000000000000	000000000000000000
3	00000000000000000	0000000000000000	00000000000000000	00000000000000000	00000000000000000	00000000000000000	00000000000000000	000000000000000000
4	00000000000000000	0000000000000000	00000000000000000	00000000000000000	00000000000000000	00000000000000000	00000000000000000	00000000000000000
5	00000000000000000	00000000000000000	00000000000000000	00000000000000000	00000000000000000	00000000000000000	00000000000000000	00000000000000000
6	00000000000000000	00000000000000000	00000000000000000	00000000000000000	00000000000000000	00000000000000000	00000000000000000	00000000000000000
7	00000000000000000	00000000000000000	00000000000000000	00000000000000000	00000000000000000	00000000000000000	00000000000000000	00000000000000000
8	00000000000000000	0000000000000000	00000000000000000	00000000000000000	00000000000000000	00000000000000000	00000000000000000	00000000000000000
9	00000000000000000	0000000000000000	00000000000000000	0000000000000000	0000000000000000	00000000000000000	0000000000000000	00000000000000000
10	0001001000110100	0010001101000101	0011010001010110	0100010101100111	0101011001111000	0110011110001001	0111100010011010	1000100110101011
11	0001001000110100	0010001101000101	0011010001010110	0100010101100111	0101011001111000	0110011110001001	0111100010011010	1000100110101011
12	0001001000110100	0010001101000101	0011010001010110	0100010101100111	0101011001111000	0110011110001001	0111100010011010	1000100110101011
13	0001001000110100	0010001101000101	0011010001010110	0100010101100111	0101011001111000	0110011110001001	0111100010011010	1000100110101011
14	0001001000110100	0010001101000101	0011010001010110	0100010101100111	0101011001111000	0110011110001001	0111100010011010	1000100110101011
15	0001001000110100	0010001101000101	0011010001010110	0100010101100111	0101011001111000	0110011110001001	0111100010011010	1000100110101011
16	0001001000110100	0010001101000101	0011010001010110	0100010101100111	0101011001111000	0110011110001001	0111100010011010	1000100110101011
<	0001001000110100	0010001101000101	0011010001010110	0100010101100111	0101011001111000	0110011110001001	0111100010011010	1000100110101011

```
7 * 8-way 16-bit multiplexor:
8 * out = a if sel == 000 d
9 * b if sel == 001 d
10 * etc.
11 * h if sel == 111 d
12 */d
13 d
14 V CHIP Mux8Way16 {d
15 V VIN a[16], b[16], c[16], d[16], d
16 V VIN a[16], f[16], g[16], h[16], d
17 V VIN sel[3]; d
18 VIN OUT out[16]; d
19 d
20 V PARTS: d
21 V // Put your code here: d
22 V Mux4Way16(a=a, b=b, c=c, d=d, sel=sel[0..1], out=abcORd); d
23 V Mux4Way16(a=e, b=f, c=g, d=h, sel=sel[0..1], out=efgORh); d
24 V Mux16(a=abcORd, b=efgORh, sel=sel[2], out=out); d
25 } d
```

```
set sel 5,
eval,
output;
set sel 6,
eval,
output;
set sel 7,
eval,
output;
set a %B0001001000110100,
set b %B0010001101000101,
set c %B0011010001010110,
set d %B0100010101100111,
set e %B0101011001111000,
set f %B0110011110001001,
set g %B0111100010011010,
set h %B1000100110101011,
set sel 0,
eval,
output;
set sel 1,
eval,
output;
set sel 2,
eval,
output;
```

```
set sel 3,
72 eval,
    output;
   set sel 4,
76 eval,
    output;
   set sel 5,
   eval,
    output;
   set sel 6,
   eval,∢
    output;
    set sel 7,
   eval,
    output;
```

Problem 2

HalfAdder.cmp											
1	П	a	-	b		sum	Τ	carry	Щel		
2	\perp	0	\perp	0	\perp	0	1	0	¤€		
3	\perp	0	\perp	1	\perp	1	1	0	¤€		
4	\perp	1		0	\perp	1	Т	0	Щel		
5	\perp	1		1	\perp	0	Т	1	Щć		
6											

```
* Computes the sum of two bits.μ4

**/μ4

9 μ4

10 CHIP HalfAdder {μ4

11 ····IN a, b; // 1-bit inputsμ4

12 ····OUT sum, // Right bit of a + bμ4

13 ······carry; // Left bit of a + bμ4

14 μ4

15 ····PARTS:μ4

16 ···// Put you code here:μ4

17 ····Xor(a=a, b=b, out=sum);μ4

18 ····And(a=a, b=b, out=carry);μ4

19 }μ4
```

```
load HalfAdder.hdl,
   output-file HalfAdder.out,
   compare-to HalfAdder.cmp,
   output-list a%B3.1.3 b%B3.1.3 sum%B3.1.3 carry%B3.1.3;
   set a 0,⊯
   set b 0, x
13 eval,¤
   output;
   set a 0,¤⊲
   set b 1, 📧
18 eval,
   output; #
   set a 1,¤
   set b 0, 🗵
  eval,¤
   output;
   set a 1,¤⊍
   set b 1, 🗵
   eval,
   output;
```

```
FullAdder.cmp
         b
                                carry |
                          sum
0
         0
                  0
                           0
                                    0
0
         0
                  1
                           1
                                    0
0
         1
                  0
                          1
                                    0
0
        1
                  1
                           0
                                   1
1
         0
                  0
                          1
                                   0
1
         0
                 1
                           0
                                   1
1
         1
                  0
                           0
                                    1
1
         1
                  1
                           1
                                    1
```

```
6  /**μθ
7  ** Computes the sum of three bits.μθ
8  **/μθ
9  μθ
10  CHIP FullAdder {μθ
11  ····IN a, b, c; // 1-bit inputsμθ
12  ····OUT sum, // Right bit of a + b + cμθ
13  ·····carry; // Left bit of a + b + cμθ
14  μθ
15  ····PARTS:μθ
16  ····// Put you code here:μθ
17  ····HalfAdder(a=a, b=b, sum=w1, carry=c1);μθ
18  ····HalfAdder(a=w1, b=c, sum=sum, carry=c2);μθ
19  ····Or(a=c1, b=c2, out=carry);μθ
20 }μθ
```

```
load FullAdder.hdl,
    output-file FullAdder.out,
   compare-to FullAdder.cmp,
    output-list a%B3.1.3 b%B3.1.3 c%B3.1.3 sum%B3.1.3 carry%B3.1.3;
    set a 0,™
   set b 0,
   set c 0,
   eval,
   output;
   set c 1,™
18 eval, m
   output; #
   set b 1, X
22 set c 0,¤
23 eval,¤
   output; #4
   set c 1,¤⊲
   eval,
   output; #
   set a 1,¤
31 set b 0,
   set c 0,
   eval,
   output; #4
    set c 1,™
    eval,
```

```
38 output; #4
39 #4
40 set b 1, #4
41 set c 0, #4
42 eval, #4
43 output; #4
44 #4
45 set c 1, #4
46 eval, #4
47 output; #4
48
```

```
* Adds two 16-bit values.
 * The most significant carry bit is ignored. ™
 */¤
CHIP Add16 {#
    IN a[16], b[16];
   OUT out[16];
   PARTS:
   // Put you code here:
   FullAdder(a=false, b=a[0],
                                       sum=out[0],
                                                    carry=c0);
                              c=b[0],
   FullAdder(a=c0,
                     b=a[1],
                              c=b[1],
                                       sum=out[1],
                                                    carry=c1);
                              c=b[2],
   FullAdder(a=c1,
                     b=a[2],
                                       sum=out[2],
                                                     carry=c2);
   FullAdder(a=c2,
                                       sum=out[3],
                     b=a[3], c=b[3],
                                                    carry=c3);
   FullAdder(a=c3,
                     b=a[4], c=b[4], sum=out[4],
                                                    carry=c4);
   FullAdder(a=c4,
                     b=a[5],
                              c=b[5],
                                       sum=out[5],
                                                     carry=c5);
   FullAdder(a=c5,
                                                    carry=c6);
                     b=a[6], c=b[6], sum=out[6],
   FullAdder(a=c6,
                     b=a[7], c=b[7], sum=out[7],
                                                    carry=c7);
   FullAdder(a=c7,
                     b=a[8],
                              c=b[8], sum=out[8],
                                                    carry=c8);
   FullAdder(a=c8,
                     b=a[9],
                              c=b[9], sum=out[9],
                                                    carry=c9);
   FullAdder(a=c9,
                     b=a[10], c=b[10], sum=out[10], carry=c10);
   FullAdder(a=c10,
                     b=a[11], c=b[11], sum=out[11], carry=c11);
   FullAdder(a=c11,
                     b=a[12], c=b[12], sum=out[12], carry=c12);
                     b=a[13], c=b[13], sum=out[13], carry=c13);
   FullAdder(a=c12,
                     b=a[14], c=b[14], sum=out[14], carry=c14);
   FullAdder(a=c13,
   FullAdder(a=c14,
                     b=a[15], c=b[15], sum=out[15], carry=c15);
```

```
load Add16.hdl,
output-file Add16.out,
compare-to Add16.cmp,
output-list a%B1.16.1 b%B1.16.1 out%B1.16.1;
set a %B0000000000000000000, 🕮
eval,
output; #
set a %B000000000000000000000, M
eval,¤
output; #4
set a %B111111111111111111, 🖂
eval,¤
output;¤↵
set a %B1010101010101010,
set b %B0101010101010101,
eval,¤
output; IK
set a %B0011110011000011,
set b %B0000111111110000,
eval,
output; #4
set a %B0001001000110100,
set b %B1001100001110110,
```

```
38 eval,¤4
39 output;¤4
```

```
load Inc16.hdl,
output-file Inc16.out,¤⊲
compare-to Inc16.cmp,
output-list in%B1.16.1 out%B1.16.1; [4]
set in %B0000000000000000, // in = 0
eval,
output; #4
set in %B111111111111111, // in = -1
eval,
output; #4
set in %B0000000000000101, // in = 5%
eval,¤
output;
set in %B11111111111111011, // in = -5
eval,
output; #4
```

Problem 3

	ALU.cmp													
1	x	у	zx	nx	zy	ny	f	: ı	no	out	zı	r	ng	←
2	00000000000000000000	11111111111111111	1		1		1			00000000000000000		1		4
3	000000000000000000	11111111111111111	1	1	1	1	1		1	000000000000000000000000000000000000000	1	0		←
4	000000000000000000	11111111111111111	1	1	1		1			1111111111111111	(0	1	4
5	00000000000000000000	11111111111111111	0		1	1	0)		00000000000000000		1		 4
6	00000000000000000000	11111111111111111	1	1			0)		1111111111111111	(0	1	4
7	00000000000000000000	11111111111111111	0		1	1	0)	1	1111111111111111	(0	1	←
8	000000000000000000000	11111111111111111	1	1			0		1	000000000000000000		1		₽
9	000000000000000000	11111111111111111	0		1	1	1		1	00000000000000000		1		[4 -
10	000000000000000000000	11111111111111111	1	1			1		1	000000000000000000001	(0		4
11	00000000000000000	11111111111111111	0	1	1	1	1		1	000000000000000000000000000000000000000	1	0		←
12	000000000000000000	11111111111111111	1	1		1	1		1	00000000000000000		1		[←
13	000000000000000000	11111111111111111	0		1	1	1			1111111111111111	(0	1	 ←
14	000000000000000000	11111111111111111	1	1			1			111111111111111	(0	1	[←
15	000000000000000000	11111111111111111	0				1			1111111111111111	(0	1	4
16	000000000000000000	11111111111111111	0	1			1		1	000000000000000000000000000000000000000	(0		4
< }	000000000000000000	11111111111111111	0			1	1		1	1111111111111111	(0	1	4
18	000000000000000000	11111111111111111	0				0)		00000000000000000		1		4
19	000000000000000000	11111111111111111	0	1		1	0)	1	1111111111111111	(0	1	4
20	0000000000010001	00000000000000011	1		1		1			00000000000000000		1		 ←
21	0000000000010001	00000000000000011	1	1	1	1	1		1	000000000000000000000000000000000000000	(0		 ←
22	0000000000010001	00000000000000011	1	1	1		1			1111111111111111	(0	1	[←
23	0000000000010001	00000000000000011	0		1	1	0)		0000000000010001	(0		 ←
24	0000000000010001	00000000000000011	1	1			0)		00000000000000011	(0		[←
25	0000000000010001	00000000000000011	0		1	1	0)	1	1111111111101110	(0	1	4
26	0000000000010001	00000000000000011	1	1			0)	1	111111111111100	(0	1	4
27	0000000000010001	00000000000000011	0		1	1	1		1	11111111111101111	(0	1	₫
28	0000000000010001	00000000000000011	1	1	0		1		1	11111111111111101	(0	1	₫
29	0000000000010001	00000000000000011	0	1	1	1	1		1	0000000000010010		0		[₽
30	0000000000010001	00000000000000011	1	1	0	1	1		1	000000000000000000000000000000000000000		0		ļ.
31	0000000000010001	00000000000000011	0		1	1	1			0000000000010000		0		ļ ĕ
32	0000000000010001	00000000000000011	1	1	0		1			000000000000000000000000000000000000000		0		[⁴
33	0000000000010001	00000000000000011	0		0		1			0000000000010100		0		ļ d
34	0000000000010001	00000000000000011	0	1	0	0	1		1	0000000000001110	(0	0	[d
35	0000000000010001	000000000000000011	1 0	I 0	I 0	1_1	'	1 J	1.	1111111111110010	L	0	1	4
36	0000000000010001	00000000000000011	a	0	a	1 0	0	a I	0	000000000000000000000001		0	l i	
37	0000000000010001	0000000000000011	10	0 1	la	1	1 4	a I	1	000000000000000000000000000000000000000		0	1 0 1 0	 4
37		00000000000000011	1 0	1 1	1 0	1 1	Τ,	9	1	000000000010011	1	0	٧	1

```
CHIP ALU {
       x[16], y[16], // 16-bit inputs
       zx, // zero the x input?
       nx, // negate the x input?
       ny, // negate the y input?
       f, // compute out = x + y (if 1) or x \& y (if 0)
       no; // negate the out output?
       ng; // 1 if (out < 0), 0 otherwise
  // Put you code here:
  Mux16(a=zeroedX, b=notX, sel=nx, out=negX);
  Mux16(a=y, b=false, sel=zy, out=zeroedy);
  Mux16(a=zeroedY, b=notY, sel=ny, out=negY);
  Add16(a=negX, b=negY, out=xPlusY);
  And16(a=negX, b=negY, out=xAndY);
  Mux16(a=xAndY, b=xPlusY, sel=f, out=funcVar);
  Not16(in=funcVar, out=negFuncVar);
  Mux16(a=funcVar, b=negFuncVar, sel=no, out=out, out[0..7]=lowOut, out[8..15]=highOut, out[15]=ng);
  Or8Way(in=lowOut, out=zero1);
  Or8Way(in=highOut, out=zero2);
```

```
load ALU.hdl,
output-file ALU2.out,
compare-to ALU.cmp,
output-list x%B1.16.1 y%B1.16.1 zx%B1.1.1 nx%B1.1.1 zy%B1.1.1
           ny%B1.1.1 f%B1.1.1 no%B1.1.1 out%B1.16.1 zr%B1.1.1
           ng%B1.1.1;
set y %B111111111111111; // y = -1
// Test0,
set zx 1,
set nx 0,
set zy 1,
set ny 0,
set f 1,
set no 0,
eval,
output;
// Test0,
set zx 1,
set nx 1,
set zy 1,
set ny 1,
set f 1,
set no 1,
eval,
output;
```

Here are just a couple of tests for the ALU, there are more tests in the ALU.tst file.

- a. less than 1296.
- b. 2 tests with 36 cases total
- c. Unlike the full ALU.cmp, the zr and ng status outputs are ignored. This is only a partial test, so the testing and implementation of the gates used the construct the ALU will be the only things needed. The nostat.tst helps concentrate on getting the correct ALU computation.
- d. 1296 and greater.
- e. 2 tests with 36 tests total
- f. To thoroughly test our ALU, we needed to include tests for the gates used to construct our ALU. We tested our 16 bit AND gate, 16 bit NOT gate, 16 bit Multiplexer, an 8 bit way OR and a regular NOT gate. We had 6 inputs and 3 outs, but if you take the powers of two, it is actually a total of 64 and 8.

Also, ALU NoStat test needed to be included because any comparison failures during the ALU.tst will be caused by errors in the handling of the ignored status outputs.